

## LAB 6: Arbitrary Waveform Generation

### Purpose

The purpose of this lab is to learn displaying waveforms we choose on oscilloscope with assistance of basys3 and VHDL. Additionally, we can change the waveforms with inputs.

### Design

On this lab, since I intend to use servo motors in my ee102 project, I choose to display PWM(pulse width modulation) method. In order to achieve square waves with this method, I used clocking method said as in lab 6 instructions. I choose clocking wizard IP and from there, I get 1 clk\_in1 input, 1 clk\_out output, and choose reset and locked ports additionally. Since, I had 2 input and 2 output in my clock. However, I almost didn't use locked one and barely used reset. The input clock frequency is 100MHz, clk\_in1. In PWM method, 120 Hz frequency is optimum value in achieving maximum productivity, however, since clocking wizard IP's minimum frequency is 10 MHz, I couldn't choose it. Hence, I didn't want to change the frequency. My output clock frequency is 100MHz, same as input.

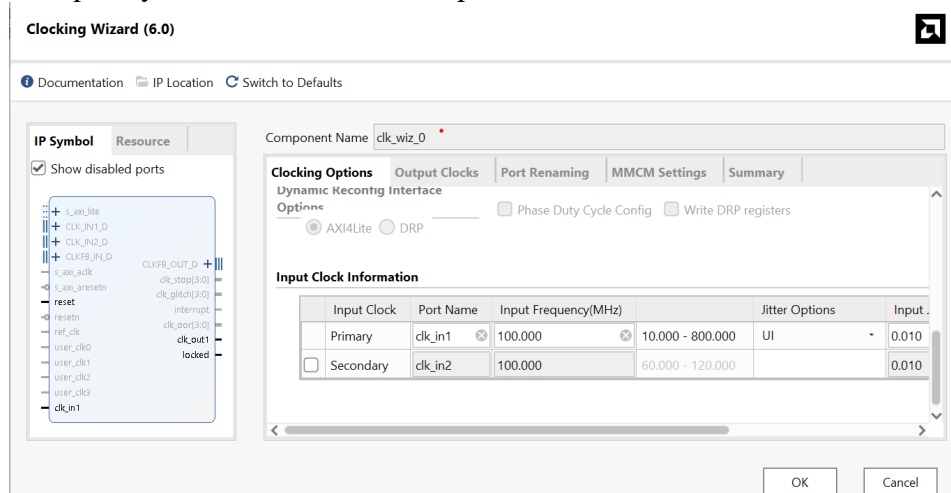


Figure 1: Clocking Wizard

CLK\_IN :input clock  
reset\_n : reset  
EN : enable  
DUTY\_CYCLE: Vector(num\_bits-1 downto 0);  
PWM\_OUT: output signal

### Methodology

On my code, on entity declaration and architecture part, I implemented the clock module I assigned and the wizard clock to each other. I keep track of the signal cycle count with counter.

This process increments the counter when EN is high and CLK\_IN is on rising edge.(Flip flop)  
The reset signal is used to asynchronously reset counter to zero. Additionally, I add the clock's information from IP sources, and wizard instantiation template. generate clock signal clk\_out1 accordingly clk\_in1. This out signal is PWM\_OUT. The duty\_cyle is a vector with length of num\_bits-1 to 0. It specifies the duty cycle of PWM signal. Duty cycle determines PWM's high percentage in comparison with its period. PWM\_OUT is the output signal. It is updated based on duty\_cycle and counter.

Additionally, the “if rising edge” process is working as initially, checking when CLK\_IN signal goes from 0 to 1(high). If rising edge detected, the statement ends with “end if”. On this part, the counter increases only the rising edges of the signal. PWM\_generator uses it to update pwm\_out signal based on duty\_cycle input and counter value, only when clock rises and EN is 1.

## Results

On this lab, my code is failed initially. I get incorrect simulation result, and the display on the oscilloscope wasn't as desired( the squares weren't so clear, and even I do autoset, the display again couldn't work). Additionally, after doing some changes, my code couldn't be synthesized. However, I get the simulation results as can be seen from figure-3 later on my works. Additionally, I get the oscilloscope waveform correctly after some differences.

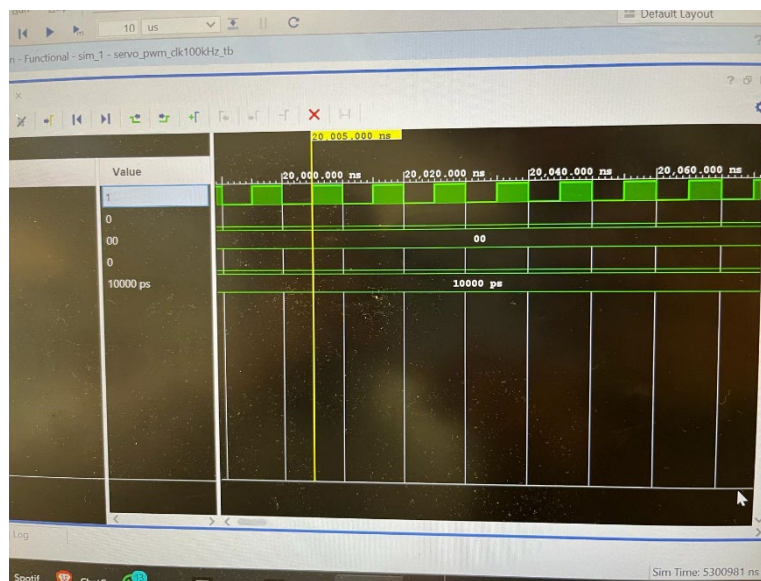


Figure-2 : Incorrect Simulation Result

 


Figure-3: Incorrect Simulation Result-2

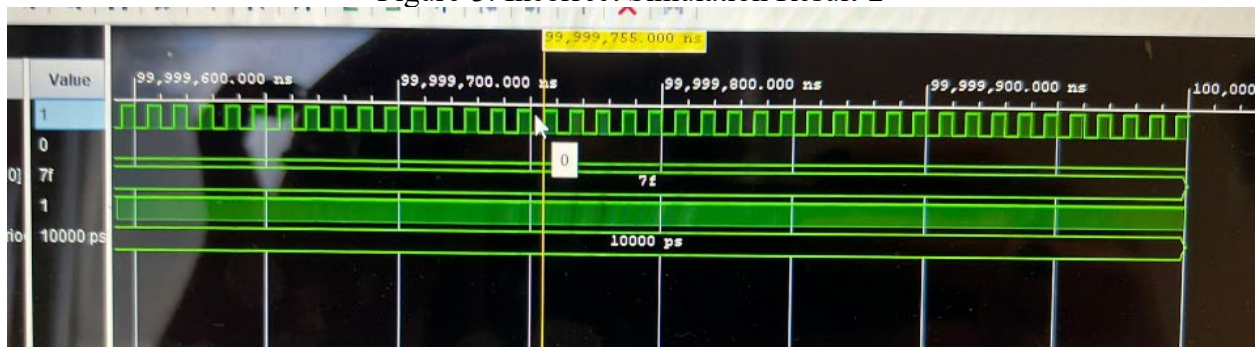


Figure-4: Correct Simulation Result

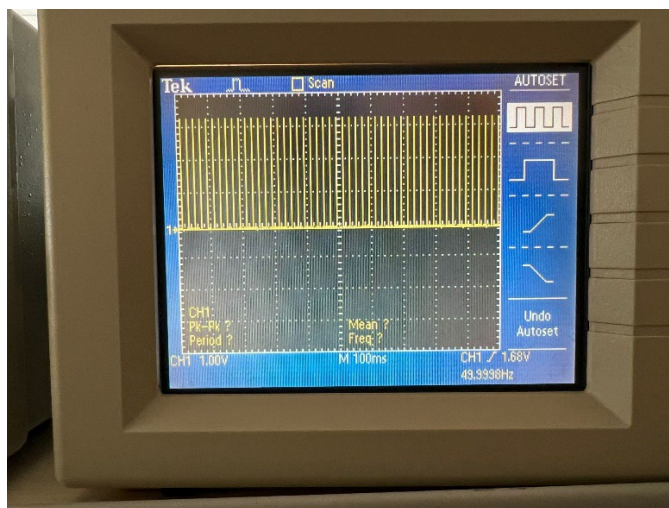


Figure-5: Oscilloscope waveform

 


Figure-6: Oscilloscope waveform 2

## Conclusion

In conclusion, on this lab, I gained knowledge about displaying PWM waveform on oscilloscope screen. Additionally, I get familiar with the concept of visualizing servo motors while working on this lab. I couldn't get the correct results initially, however, the results finally be as I desired. The reason why my code didn't work initially is that I couldn't assign the clock wizard module in correct place. I used the module but didn't add to my results, and didn't assign the ports on it. Also, I faced with some problems on my constraint file, while connecting the oscilloscope with fpga.

## References

<https://digilent.com/reference/programmable-logic/basys-3/reference-manual>  
<https://vhdl.lapinoo.net/testbench/>  
[https://github.com/Budea-Patrick/PWM-VHDL/tree/main/pwm.srcs/sources\\_1](https://github.com/Budea-Patrick/PWM-VHDL/tree/main/pwm.srcs/sources_1)  
<https://stackoverflow.com/questions/29945327/square-waveform-generation>

## Appendices

### Main.pwm

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use IEEE.math_real.all;
ENTITY main.pwm is
    generic(
        num_bits : INTEGER := 12
    );
    port(
        CLK_IN  : IN STD_LOGIC;
        reset_n : IN STD_LOGIC;
```

```

    EN : IN STD_LOGIC;
    DUTY_CYCLE: IN STD_LOGIC_VECTOR(num_bits-1 downto 0);
    PWM_OUT: OUT STD_LOGIC
);
END main.pwm;
ARCHITECTURE RTL OF main.pwm is
component clk_wiz_0
port
(
    clk_out1 : out std_logic;
    clk_in1 : in std_logic
);
end component;
signal counter: UNSIGNED(num_bits-1 downto 0);
begin
your_instance_name : clk_wiz_0
    port map (
        clk_out1 => PWM_OUT,
        clk_in1 => CLK_IN
    );
count_proc: process(CLK_IN,reset_n)
begin
    if(reset_n = '0') then
        counter <= (others => '0');

    elsif rising_edge(CLK_IN) then
        if (EN = '1') then
            counter <= counter + 1;
        else
            counter <= counter;
        end if;
    end if;
end process count_proc;
PWM_generator: process(CLK_IN,reset_n)
begin
    if(reset_n = '0') then
        PWM_OUT <= '0';
    elsif rising_edge(CLK_IN) then
        if (EN = '1') then
            if (counter < unsigned(DUTY_CYCLE)) then
                PWM_OUT <= '1';
            else
                PWM_OUT <= '0';
            end if;
        else
            PWM_out <= '0';
        end if;
    end if;
end process PWM_generator;
end architecture RTL;

```

```

        end if;
    end if;
end process PWM_generator;
END RTL;

```

### **Tb\_main.pwm**

```

library ieee;
use ieee.std_logic_1164.all;
entity tb_main.pwm is
end tb_main.pwm;
architecture tb of tb_main.pwm is
    component main.pwm
        port (CLK_IN    : in std_logic;
              reset_n   : in std_logic;
              EN        : in std_logic;
              DUTY_CYCLE : in std_logic_vector (num_bits-1 downto 0);
              PWM_OUT    : out std_logic);
    end component;
    signal CLK_IN    : std_logic;
    signal reset_n   : std_logic;
    signal EN        : std_logic;
    signal DUTY_CYCLE : std_logic_vector (num_bits-1 downto 0);
    signal PWM_OUT    : std_logic;
    constant TbPeriod : time := 1000 ns;
    signal TbClock : std_logic := '0';
    signal TbSimEnded : std_logic := '0';
begin
    dut : main.pwm
    port map (CLK_IN    => CLK_IN,
              reset_n   => reset_n,
              EN        => EN,
              DUTY_CYCLE => DUTY_CYCLE,
              PWM_OUT    => PWM_OUT);
    TbClock <= not TbClock after TbPeriod/2 when TbSimEnded /= '1' else '0';
    CLK_IN <= TbClock;
    stimuli : process
    begin
        EN <= '0';
        DUTY_CYCLE <= (others => '0');
        reset_n <= '1';
        wait for 100 ns;
        reset_n <= '0';
        wait for 100 ns;
        wait for 100 * TbPeriod;
        TbSimEnded <= '1';
        wait;
    end process;
end tb_main.pwm;

```

```
    end process;
end tb;
configuration cfg_tb_main.pwm of tb_main.pwm is
    for tb
        end for;
end cfg_tb_main.pwm;
```